

### XOR TRUTH TABLE -

M	B	$M \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$$\Rightarrow B \oplus 0 = B$$

$$\& B \oplus 1 = \overline{B}$$

1) When  $M=0$ , value of B is passed as it is from the XOR gate;  $C_{in}$  for first full adder is 0 and carry generated is passed on to next full adders & hence process is repeated until the addition of the 2 4-bit numbers.

2) When  $M=1$ , value of complement of B is passed as it is from the XOR gate;  $C_{in}$  for first full adder is 1 then the operation at full adder will be  $\overline{B} + 1 + A$

2's complement of B without sign bit

which is equivalent to  $A - B$

which <sup>finally</sup> results in subtraction of the 2 4-bit numbers.